


Power Amplifiers

Class B

Class AB

Class B

The circuit


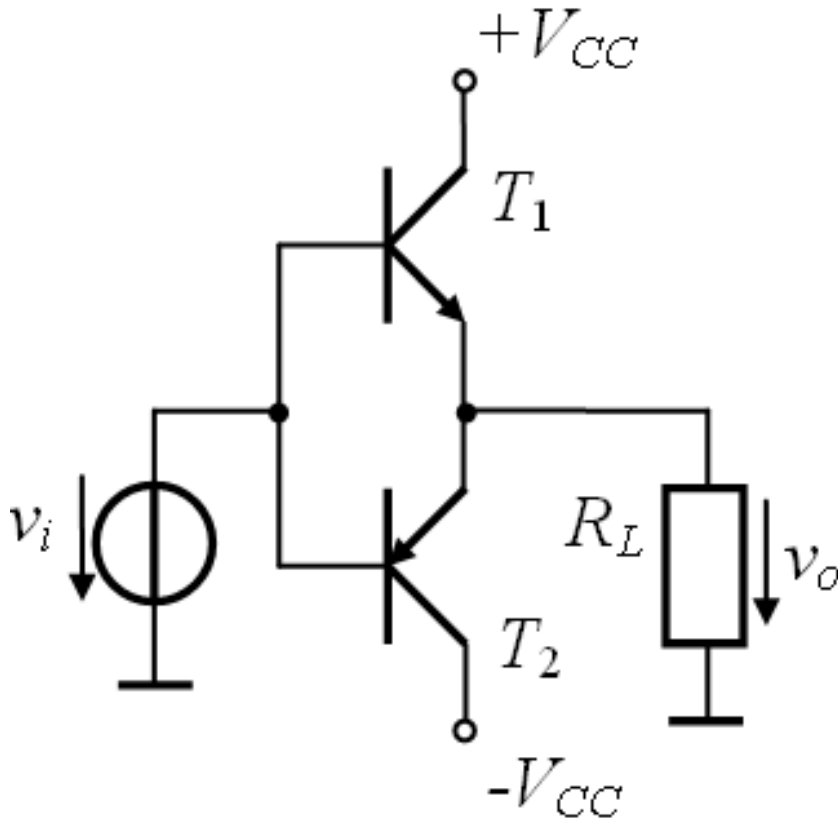


each transistor
conducts for a half of
every signal period

complementary pair
push-pull arrangement

Operation

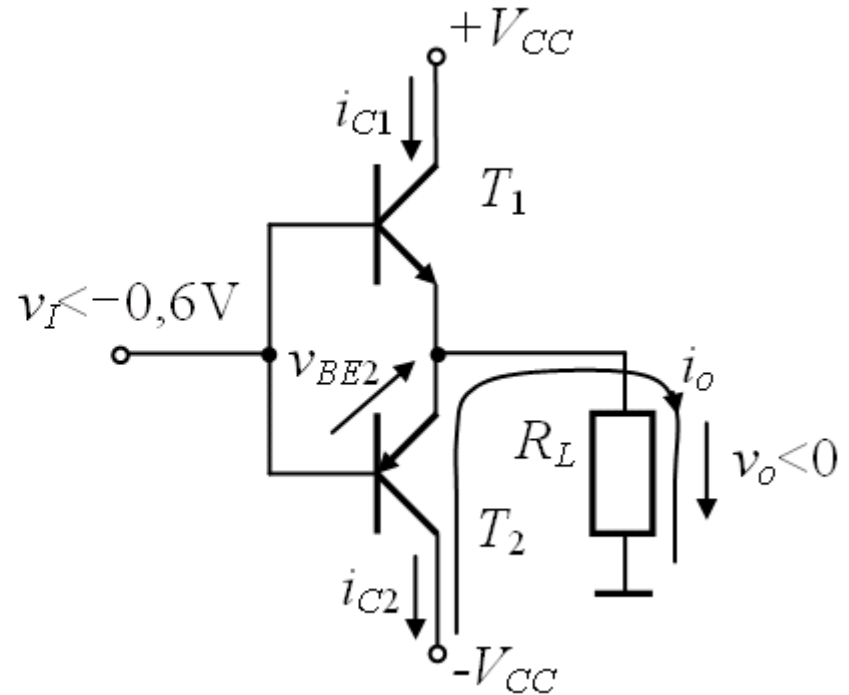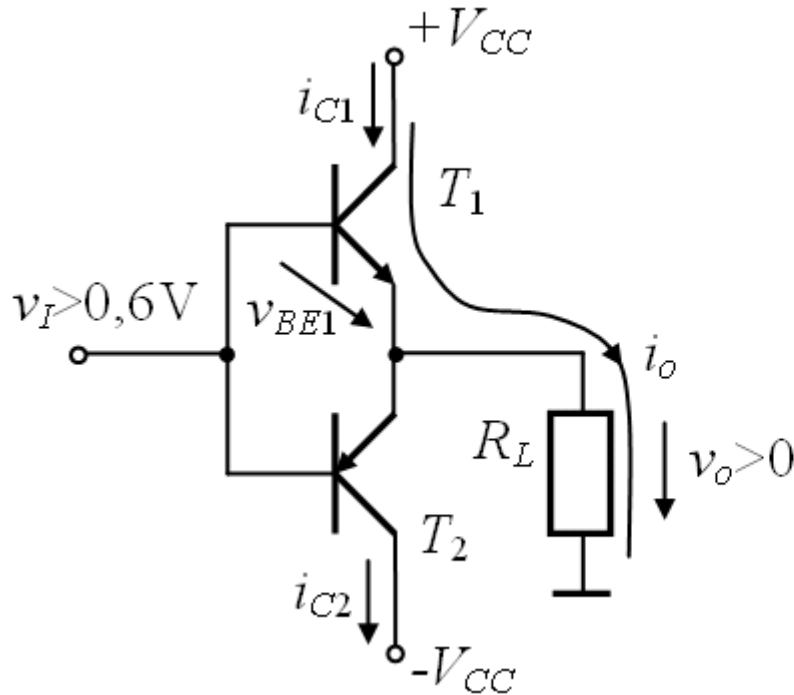$v_I \in (-0.7V; +0.7V)$ $T_1 - (off), T_2 - (off)$ $v_O = 0V$



$v_I \geq 0.7V$ $T_1 - (on), T_2 - (off)$

$$v_O = v_I - v_{BE1} = v_I - 0.7V$$

$$i_O > 0 \quad i_{C1} = i_O \quad i_{C2} = 0$$

$$v_{Omax} = V_{CC} - V_{CEsat} \approx V_{CC}$$

$v_I \leq -0.7V$ $T_1 - (off), T_2 - (on)$

$$v_O = v_I - v_{BE2} = v_I + 0.7V$$

$$i_O < 0 \quad i_{C2} = -i_O \quad i_{C1} = 0$$


$$v_{Omin} = -V_{CC} + V_{CE1sat} \approx -V_{CC}$$

Voltage transfer characteristic (VTC)

$$v_I \geq 0.7V \quad T1 - (on), T2 - (off)$$
$$v_O = v_I - 0.7V$$

$$v_{o\max} = V_{CC} - V_{CEsat} \approx V_{CC}$$


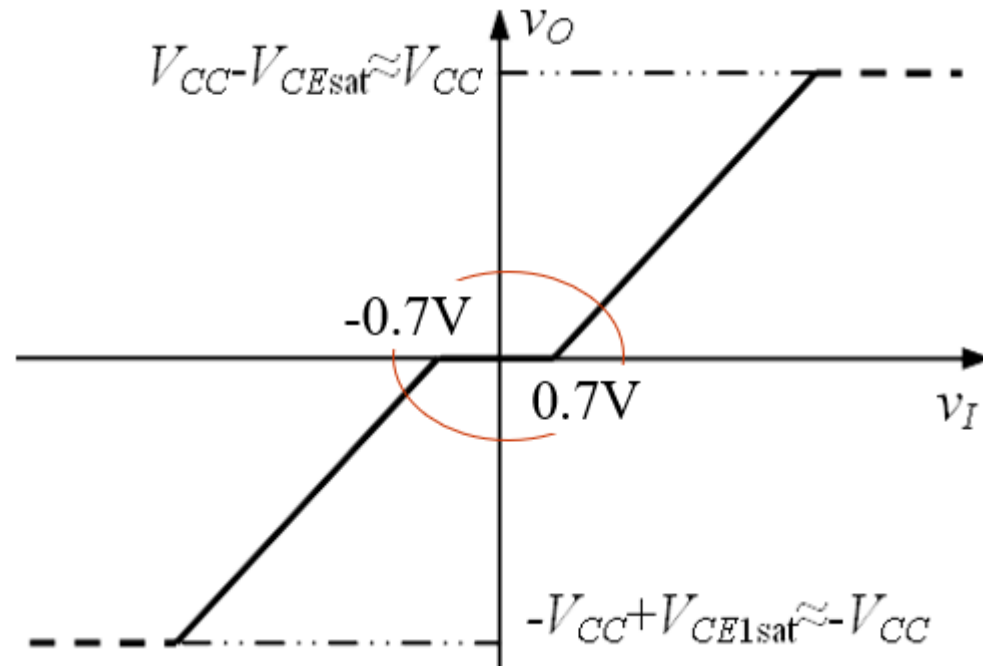
$$v_I \in (-0.7V; 0.7V)$$
$$T1 - (off), T2 - (off)$$
$$v_O = 0V$$



$$v_I \leq -0.7V \quad T1 - (off), T2 - (on)$$
$$v_O = v_I + 0.7V$$

$$v_{o\min} = -V_{CC} + V_{CE1sat} \approx -V_{CC}$$

Crossover distortions


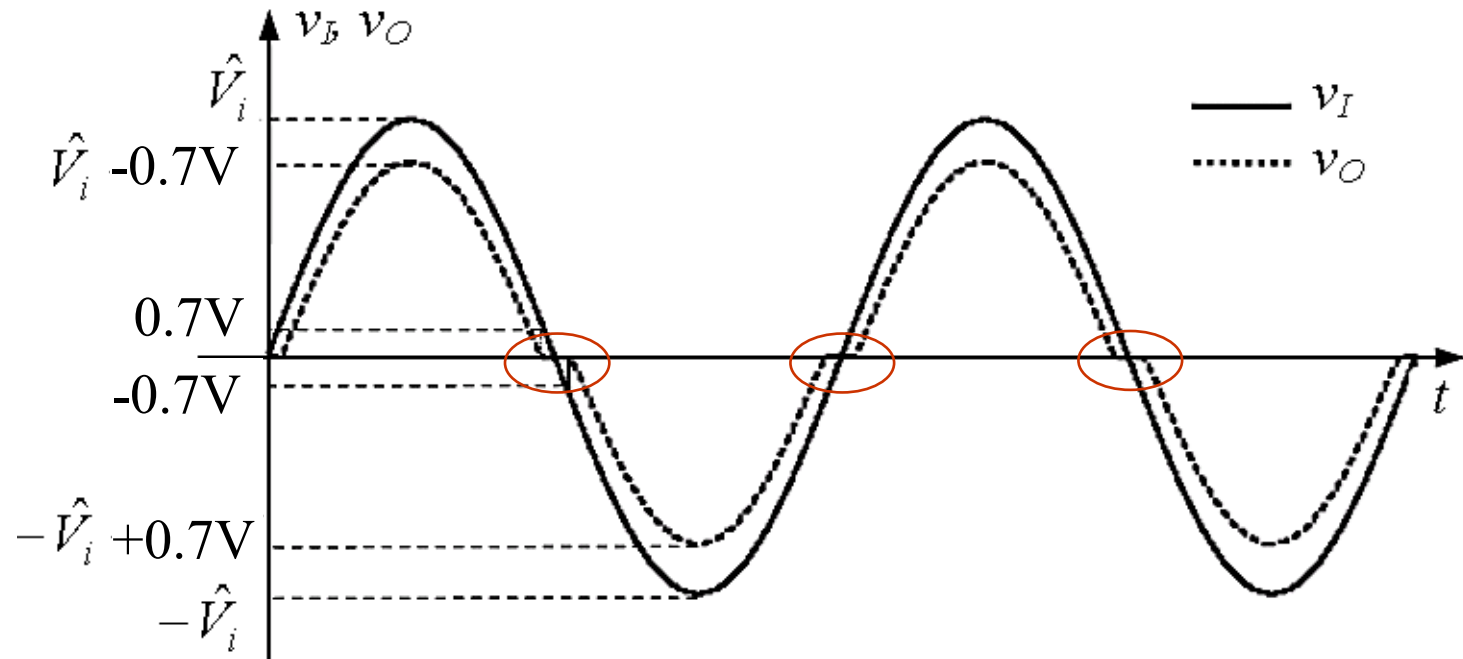
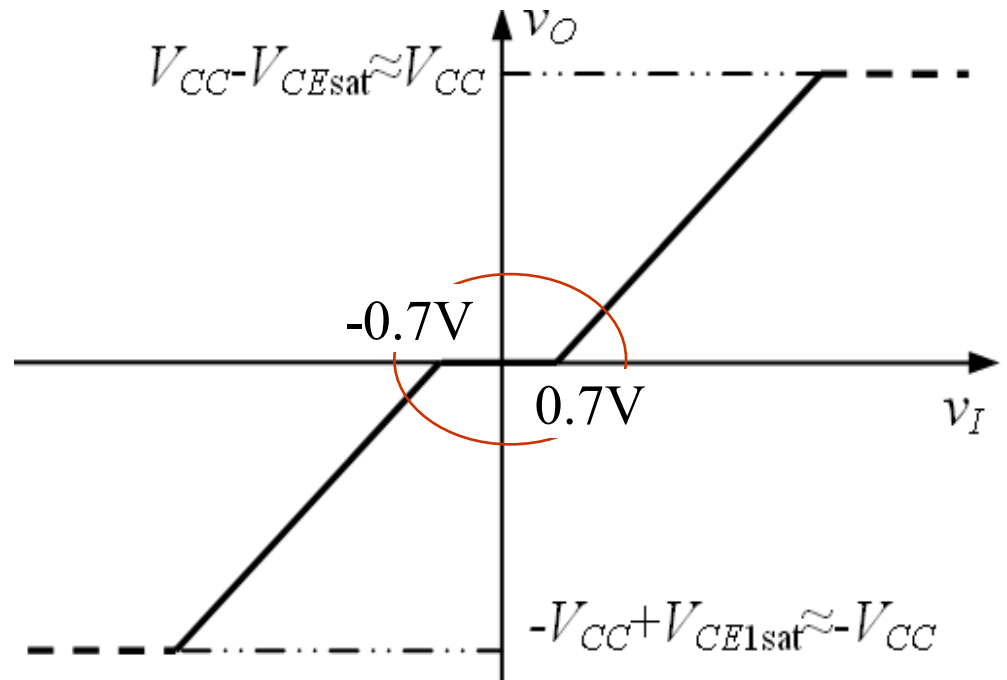


Waveforms

Assume the signal magnitude sufficiently high to neglect the crossover distortions.

$$v_o(t) = \hat{V}_o \sin \omega t$$

$$\hat{V}_o = V_{CC}$$

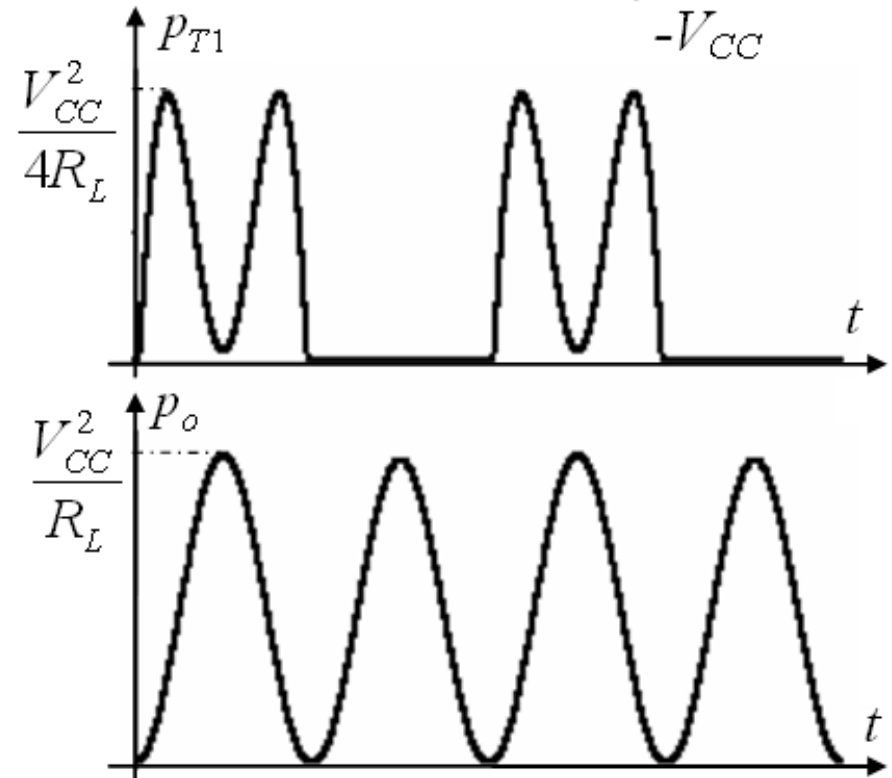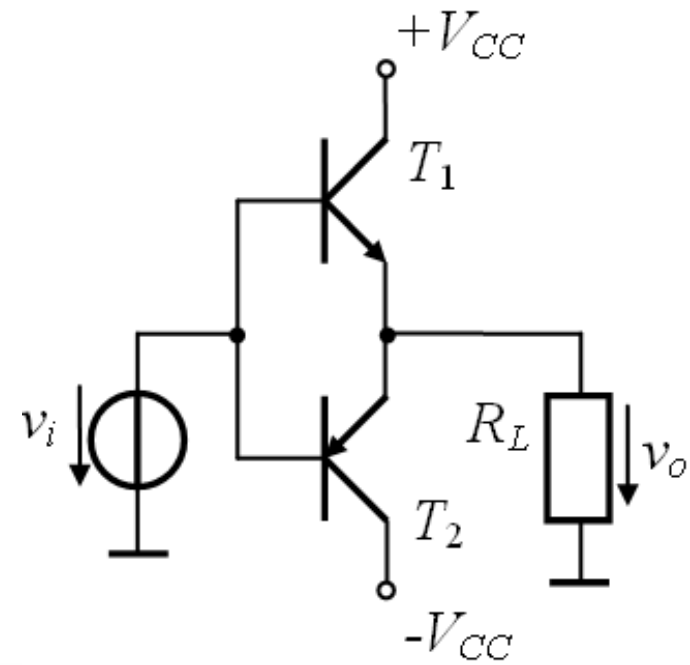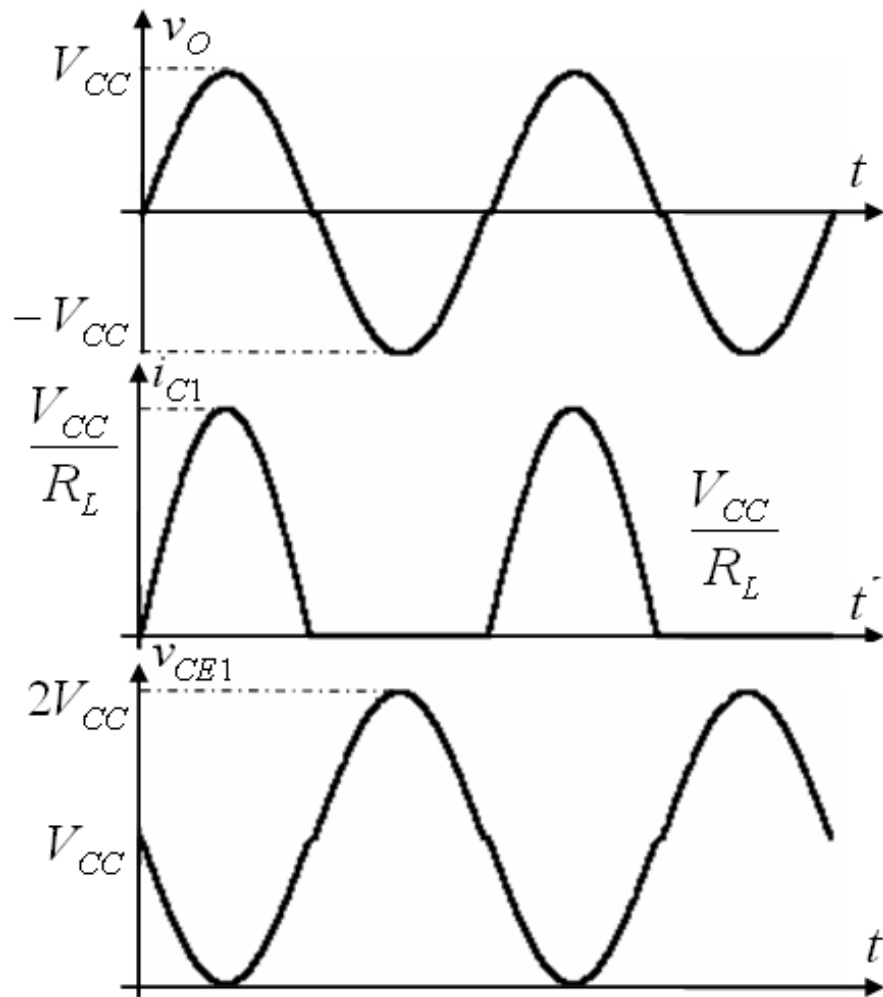

Powers. Efficiency

$$\eta = \frac{P_O}{P_{PS}}$$

$$P_{PS}^+ = \frac{1}{T} \int_0^T V_{CC} i_{C1}(t) dt = \frac{1}{T} \int_0^{T/2} V_{CC} \frac{\hat{V}_o \sin \omega t}{R_L} dt$$

$$P_{PS}^+ = \frac{1}{T} \frac{V_{CC} \hat{V}_o}{R_L} \int_0^{T/2} \sin \frac{2\pi}{T} t dt$$

$$P_{PS}^+ = \frac{1}{\pi} \frac{V_{CC} \hat{V}_o}{R_L}$$

$$P_{PS} = P_{PS}^+ + P_{PS}^- = \frac{2}{\pi} \frac{V_{CC} \hat{V}_o}{R_L}$$

For $\hat{V}_o = V_{CC}$

$$P_{PS\max} = \frac{2}{\pi} \frac{V_{CC}^2}{R_L}$$

$$P_O = V_{Orms} I_{Orms} = \frac{\hat{V}_o^2}{2R_L}$$

For $\hat{V}_o = V_{CC}$

$$P_{O\max} = \frac{V_{CC}^2}{2R_L}$$

Average efficiency:

$$\eta = \frac{P_O}{P_{PS}} = \frac{\hat{V}_o^2}{2R_L} \frac{\pi}{2} \frac{R_L}{V_{CC} \hat{V}_o} = \frac{\pi}{4} \frac{\hat{V}_o}{V_{CC}}$$

Maximum average efficiency:

for $\hat{V}_o = V_{CC}$

$$\eta_{\max} = \frac{\pi}{4} = 78.5\%$$

The amplifying transistor

$$P_T = \frac{1}{2}(P_{PS} - P_O)$$

$$P_T = \frac{1}{2}(P_{PS} - P_O) = \frac{1}{\pi} \frac{V_{CC} \hat{V}_o}{R_L} - \frac{\hat{V}_o^2}{4R_L}$$

Maximum efficiency: $\hat{V}_o = V_{CC}$ $P_T = \frac{1}{\pi} \frac{V_{CC}^2}{R_L} - \frac{\hat{V}_{CC}^2}{4R_L} = 0.068 \frac{\hat{V}_{CC}^2}{R_L}$

What is the maximum average power dissipated by a transistor depending on the output voltage magnitude?

$$\frac{dP_T}{d\hat{V}_o} = 0 \quad \Rightarrow \quad \hat{V}_o = \frac{2}{\pi} V_{CC} = 0.64V_{CC}$$

Maximum average power: $\hat{V}_o = 0.64V_{CC}$ $P_{Tmax} = \frac{1}{\pi^2} \frac{V_{CC}^2}{R_L} \approx 0.1 \frac{V_{CC}^2}{R_L}$

Maximum instantaneous power: $\hat{V}_o = V_{CC}$ $p_{Tmax} = \frac{1}{4} \frac{V_{CC}^2}{R_L} = 0.25 \frac{V_{CC}^2}{R_L}$


$$i_{Cmax} = \frac{V_{CC}}{R_L} \quad v_{CEmax} = 2V_{CC}$$

OPTIONAL

Class AB

- Crossover distortion, specific to class B amplifier can be virtually eliminated

Class AB Amplifier. Basic Circuit

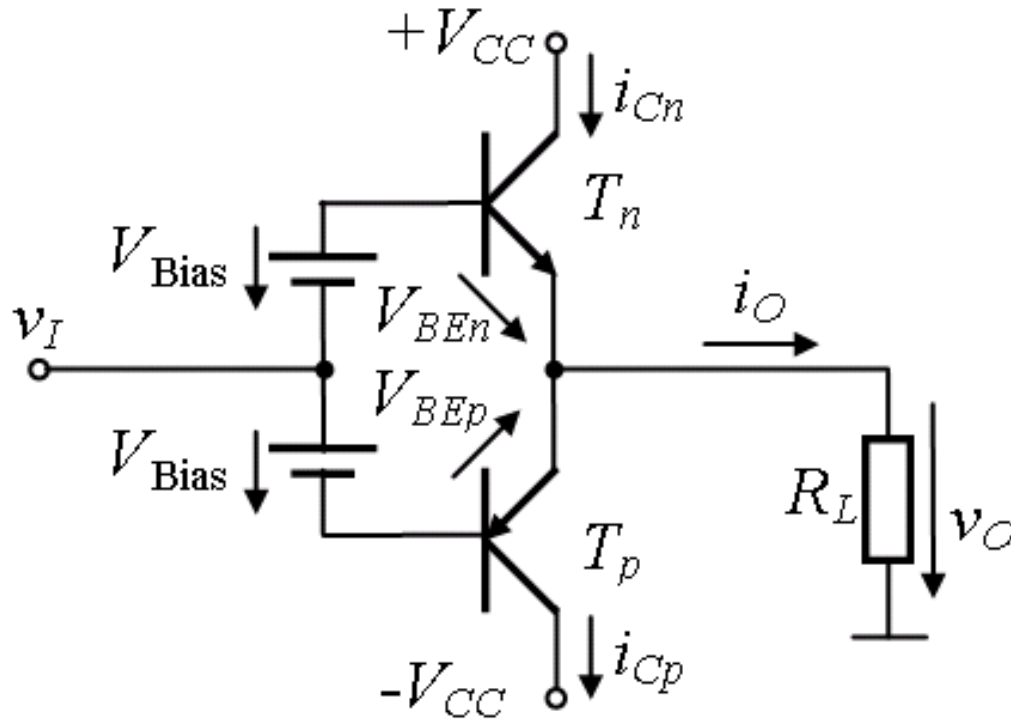

- biasing the complementary output transistors at a small output current

$$V_{Bias} \approx 0.7V$$



$$I = I_S e^{\frac{V_{Bias}}{V_T}}$$

v_I - positive

$$v_O(t) = v_I(t) + V_{Bias} - V_{BE n} \approx v_I(t)$$

v_I - negative
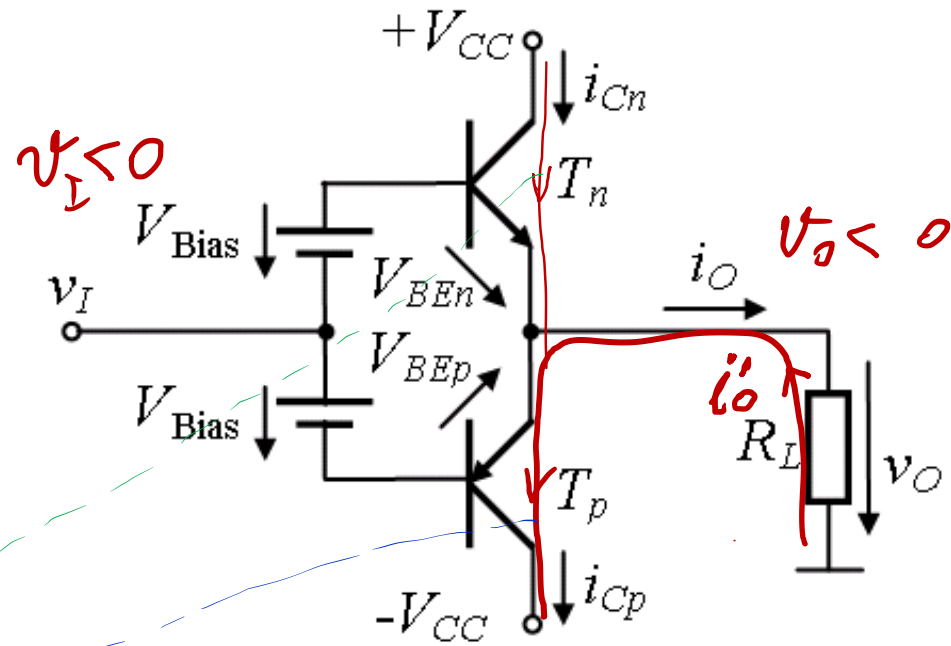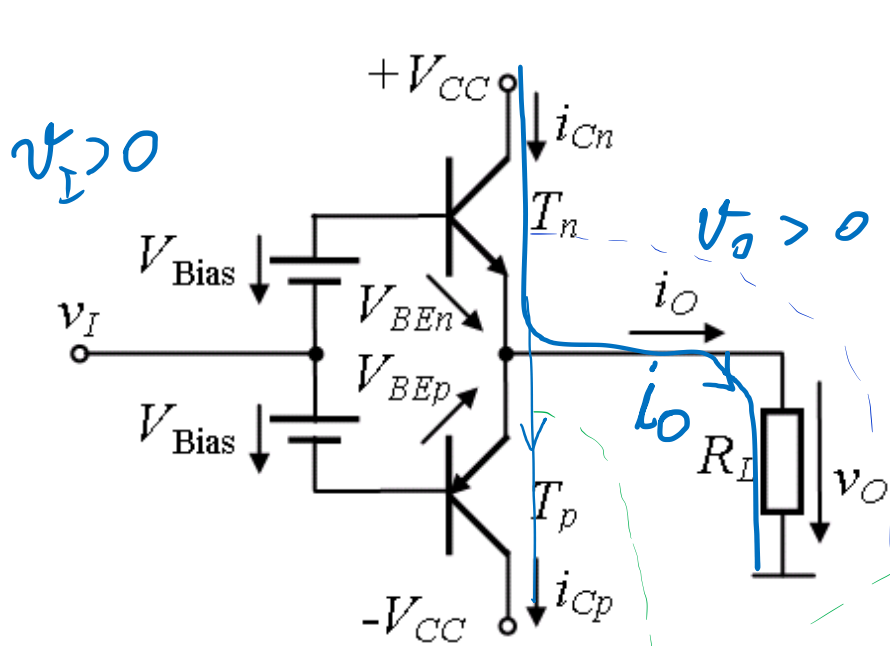
$$v_O(t) = v_I(t) - V_{Bias} - V_{BE p} \approx v_I(t)$$



$$v_I > 0, v_O > 0$$

$$i_{Cn} = i_O + i_{Cp}$$

T_n provides the output current

$$T_n - (C); T_p - (C)$$

$$v_I < 0, v_O < 0$$

$$i_{Cp} = i_O' + i_{Cn}$$



T_p provides the output current

$$T_p - (C) \quad T_n - (C)$$

Voltage Transfer Characteristic (VTC)


$$v_O(t) = v_I(t)$$

$$v_O(t) = v_I'(t) + 0.7V$$

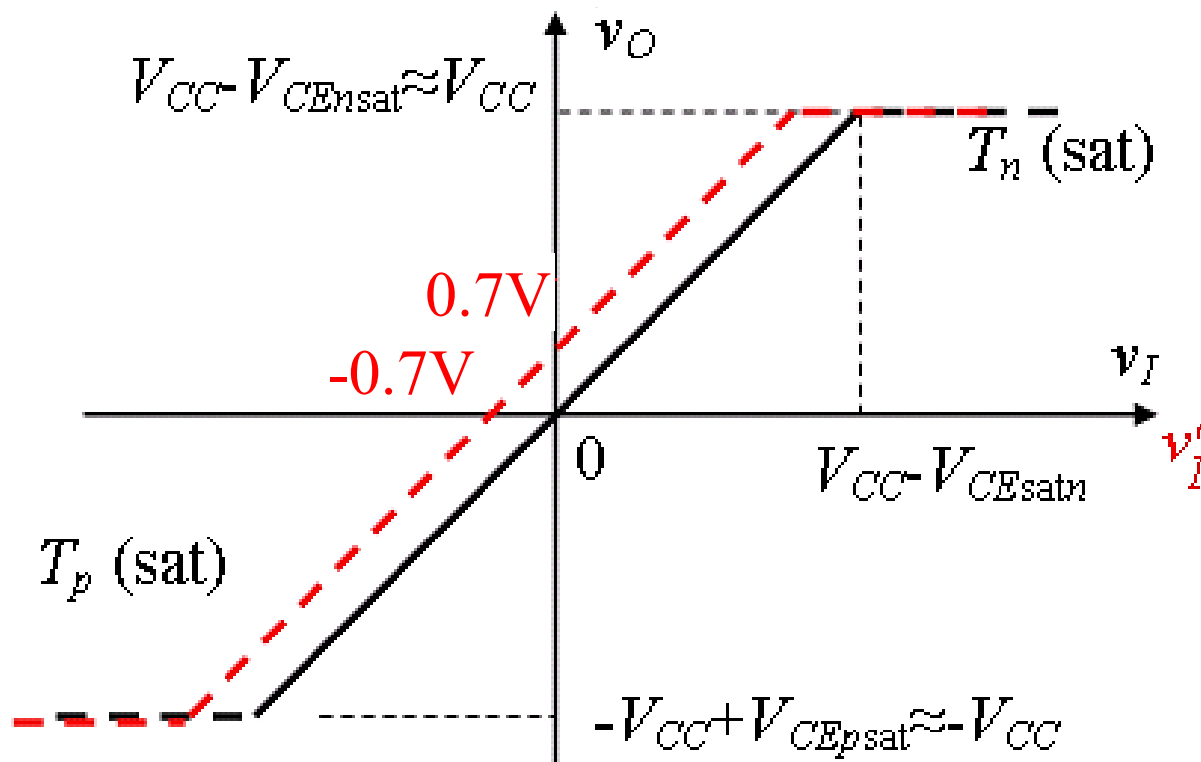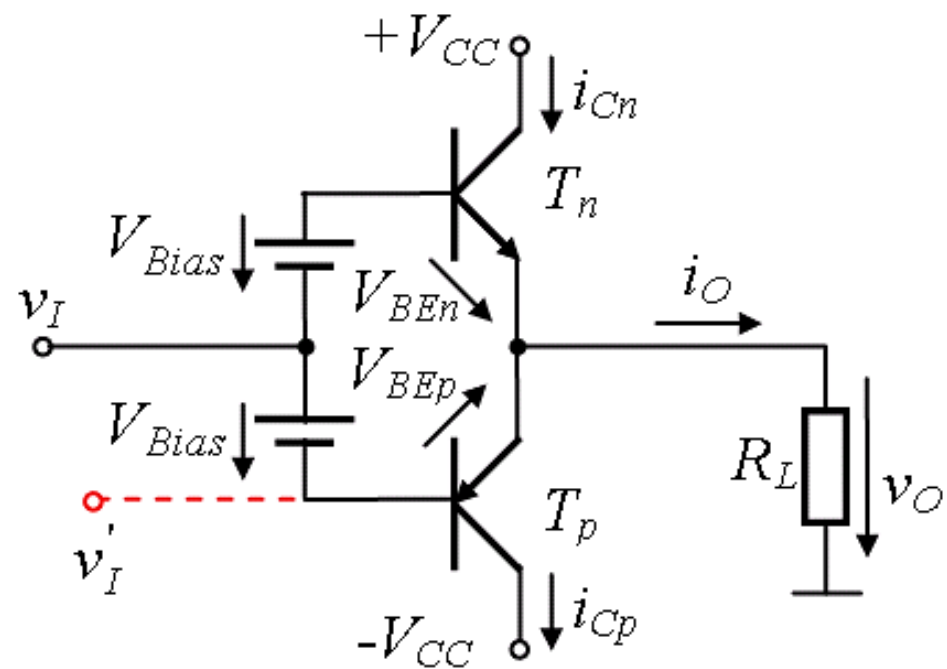

Solutions to generate V_{bias} ?

Biasing using Diodes

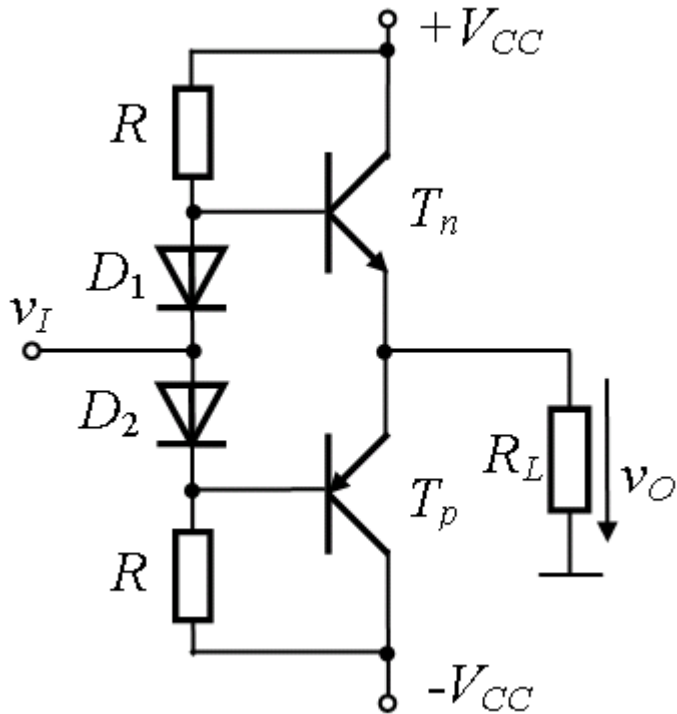


R should allow the currents in the diodes and in the bases of the transistors, even for maximum output current

$$V_{CC} = +15\text{V} \quad \hat{V}_O = 8\text{V} \quad \beta = 50$$

$$R_L = 100\Omega, \quad I_{D1} = 1.5\text{mA}$$

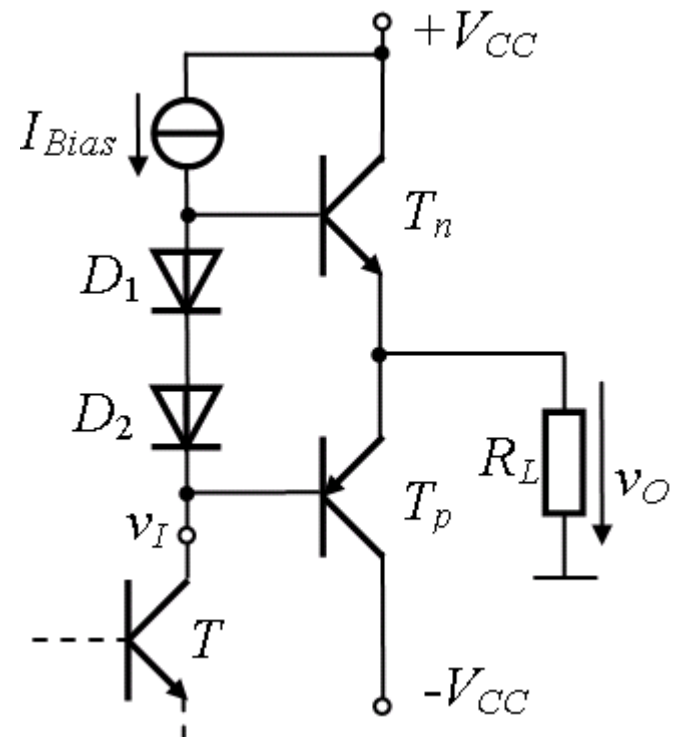
$$R = ?, \quad I_R = ? \quad (\text{each } R)$$




T is the driver transistor from previous amplifier stage

Biasing using V_{BE} Multiplier

Optional

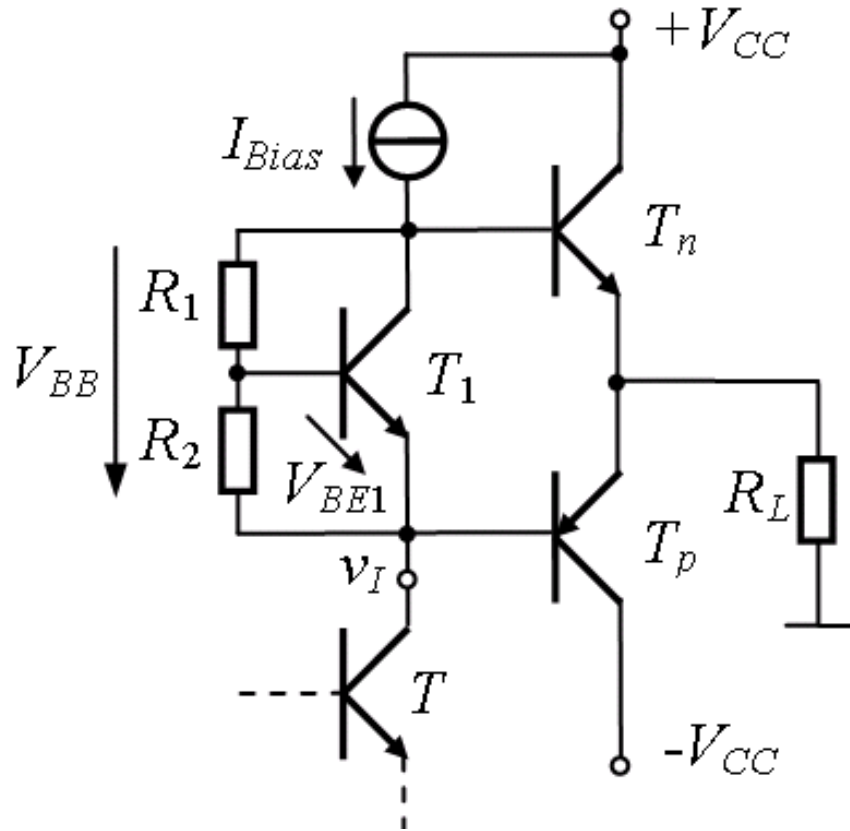
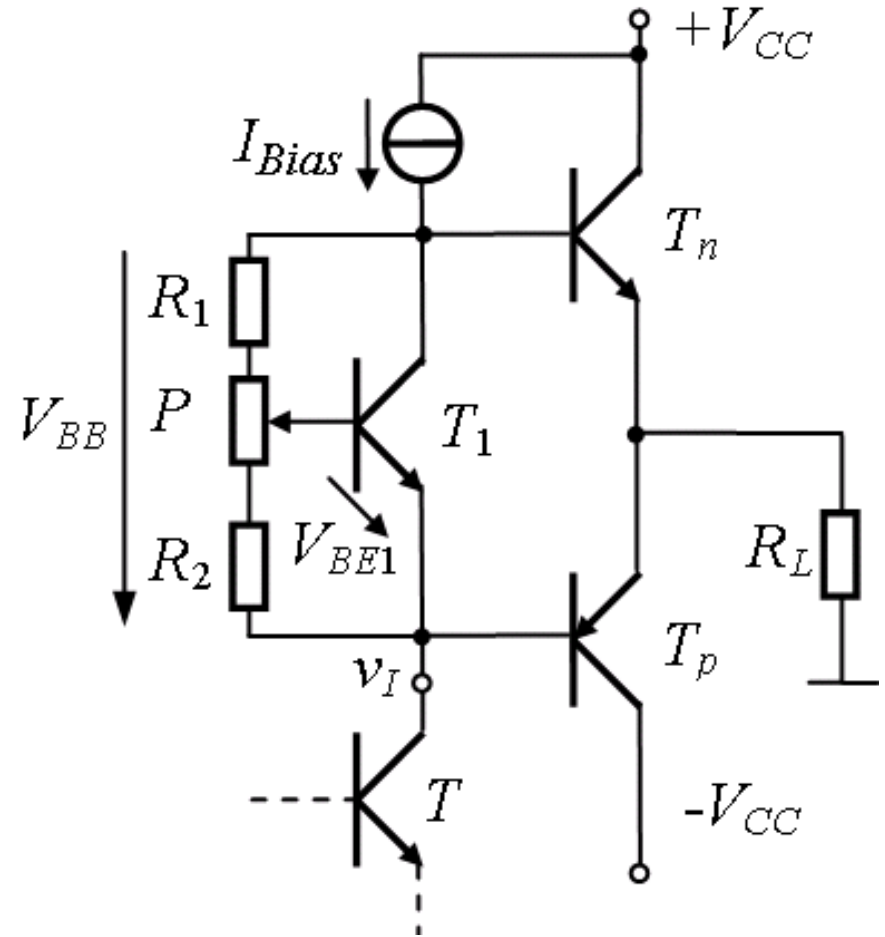
$$V_{BB} = \left(1 + \frac{R_1}{R_2}\right) V_{BE1}$$




Short-Circuit Protection

Protection against the effect of short-circuiting the output

Elements for short-circuit protection:

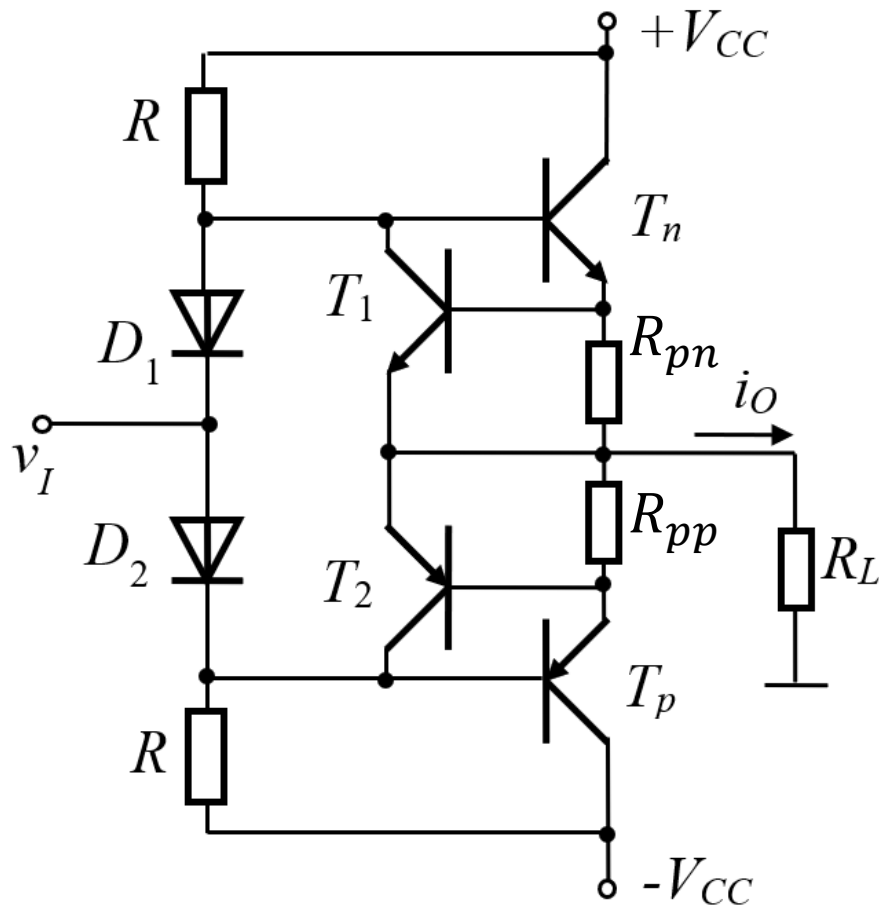- T_1, R_{pn} – for $v_o > 0V$
- T_2, R_{pp} – for $v_o < 0V$




When $v_o > 0V$

➤ If $R_{pn}i_o < 0.6V$
 T_1 – (off); $i_o = \frac{v_o}{R_L}$

➤ If i_o increases,
 when $R_{pn}i_o = 0.7V$


$$T_1 \text{ – (on); } i_{Omax} = \frac{V_{BE1,on}}{R_{pn}} = \frac{0.7V}{R_{pn}}$$

Short-Circuit Protection

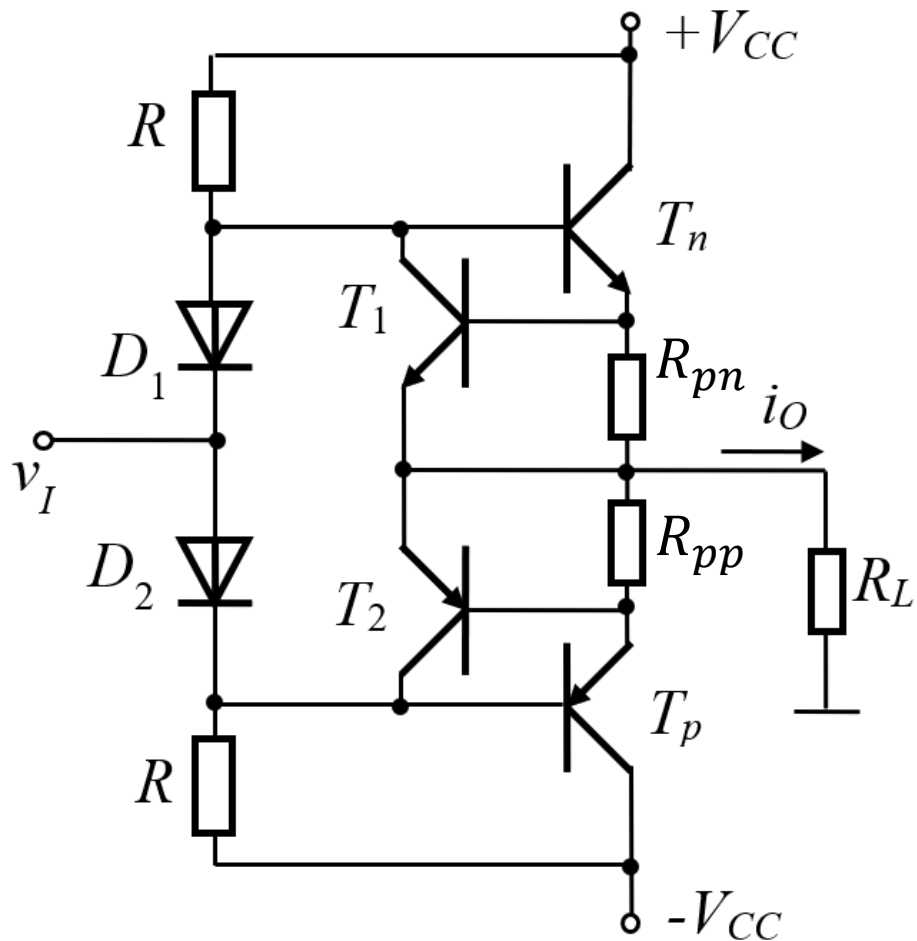

- Effective in ensuring device safety
- Disadvantage: under normal operation up to 0.7V appears across each protection resistor. The voltage swing will be reduced by that much, in each direction
- Negative feedback, protection of the output transistor against thermal runaway

Optional

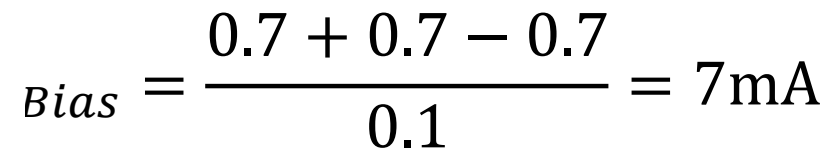


C - in the bases of T_n
and T_p :


$$i_{O\max}=0.7\text{A}$$

Use of Compound Transistors with Higher Current Gain


- Necessary for high output currents

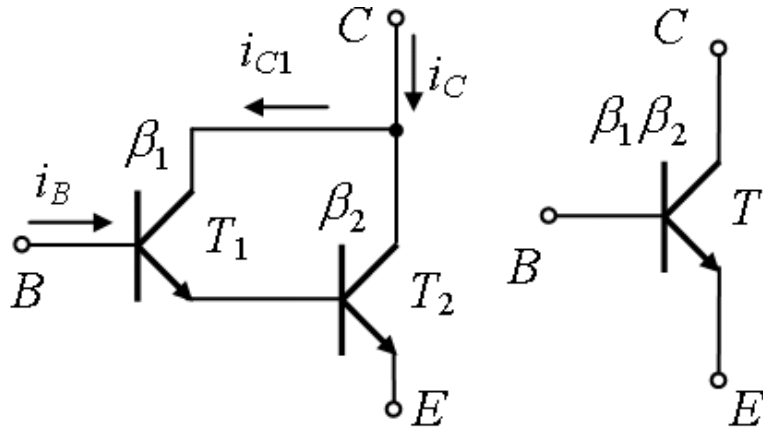


The Darlington *nnp* configuration

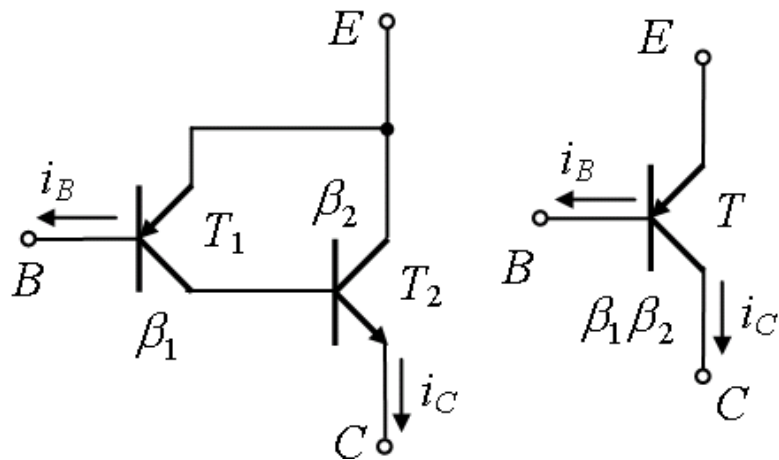


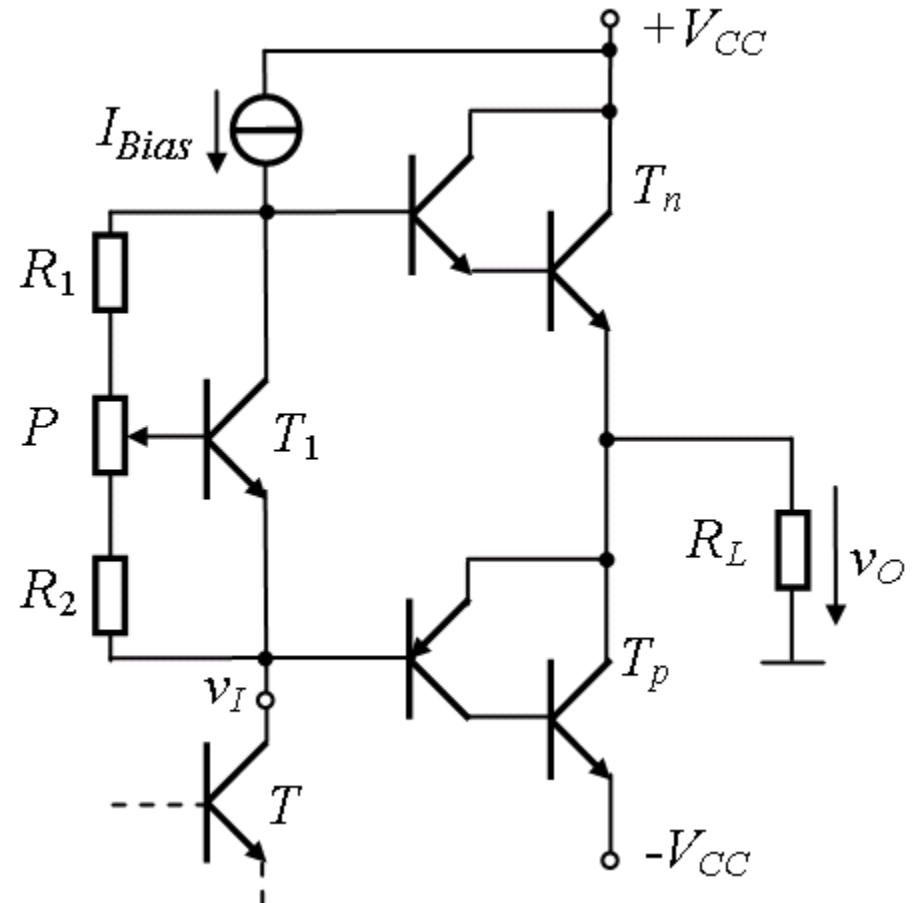The compound *pnp* configuration preferred in IC



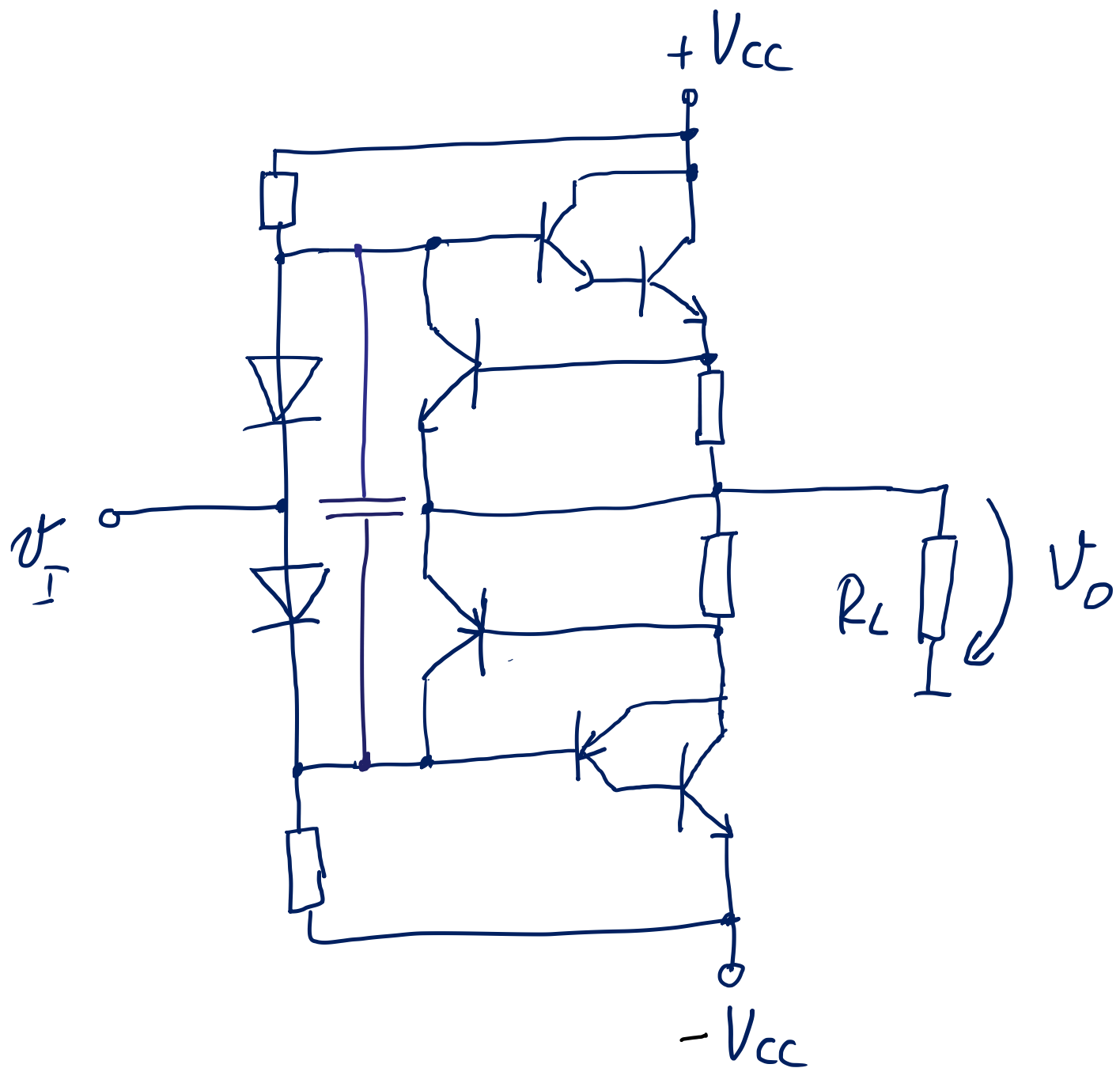

Problem

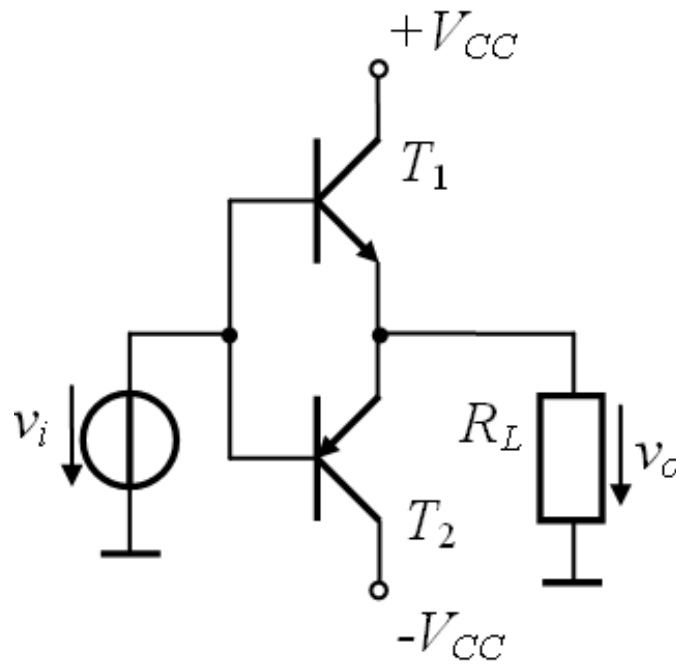

$$\pm V_{CC} = \pm 15\text{V}$$

$$R_{L1} = 500\Omega$$

$$R_{L2} = 50\Omega$$

- a)** What is the expression $v_o(v_i)$ for $v_i \in [-10\text{V}; 10\text{V}]$? Plot the $v_o(v_i)$ VTC. What is the operating class of this amplifier? What is the maximum theoretical average efficiency?
- b)** Plot $v_o(t)$ for: (1) $v_i(t) = 0.2\sin\omega t$ [V]; (2) $v_i(t) = 10\sin\omega t$ [V].
- c)** For $v_i(t) = 10\sin\omega t$ [V], $v_o(t)$ can be well approximated by a sinewave (neglecting crossover distortions). Compute: the average output power, the average power consumption, and the average efficiency of the stage. Plot the collector-emitter voltage and collector current for T_1 and T_2 .
- d)** Propose a solution to eliminate crossover distortion.